

Lab report: Experimenting with digital meter assembly

Tiankai Ma PB21000030

November 8, 2022

Abstract

Digital meter plays a more and more important role in electrical experiments, understanding how it works helps improve experiment design and reduce the risk of accidents. This report will introduce the working principle of the digital meter and the assembly of the digital meter and gives a brief description of how its impact on the measuring system.

Keywords: Digital meter, Electrical experiments, Measuring system

Introduction

Digital meter

Compared to the analog meter, the digital meter has more advantages. It is more accurate, more stable, and more convenient to use. In this experiment, we are going to expand its features to adapt it for voltage, current, and resistance measurement. More importantly, by experimenting with how measuring equipment impacts measured results, we will learn how to design a better measuring system.

Features of digital meter:

Compared to pointer meters, digital meters have the following excellent characteristics.

- High accuracy and resolution
- Digital voltmeter has a high input impedance

- Fast measurement rate
- Automatic polarity discrimination
- Digital direct reading of all measurements
- High overload resistance

DC Voltage Measurement Circuit

The range of DC voltage measurement can be extended by adding a voltage divider circuit(voltage divider)in front of the digital voltmeter head. As shown in Figure 1, U_0 is the range of the digital voltmeter head (e.g. $200mV$), r is its internal resistance (e.g. $10M\Omega$), r_1 and r_2 are the voltage divider resistors, and U_{i0} is the extended range.

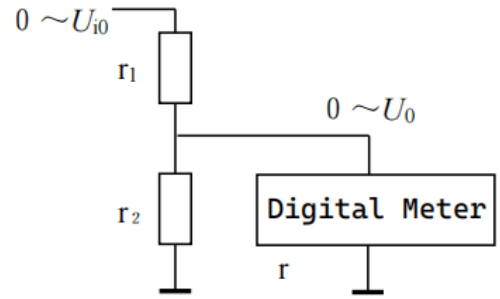


Figure 1: Single range voltage divider circuit

If we have $r \gg r_2$, the impact of r could be ignored, we have the following equation:

$$\frac{U_0}{U_{i0}} = \frac{r_2}{r_1 + r_2}$$

The extended range is $U_{i0} = U_0 \cdot \frac{r_1 + r_2}{r_2}$.

Analysis of the measurement error

During measurement, the error comes mainly from two aspects: one is introducing the meter inside the circuit, which stays the same throughout the measurement, the is considered a system error; the other is caused by the assembled meter, which is considered a random error.

System error:

Since the internal resistance of the voltmeter is not infinite, using a voltmeter to measure the voltage across the circuit components will affect the measurement results. We use the measurement circuit shown in Figure 2 to analyze the measurement error of the assembled meter and accordingly study the effect of the measuring instrument on the measurement results.

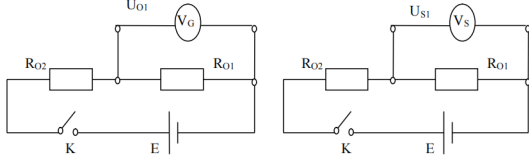


Figure 2: Comparison of the measurement error of the assembled meter

The measured data should be expressed in the following equation:

$$\begin{cases} U_{s1} = E \cdot \frac{R_{o1}}{R_{o1} + R_{o2}} \\ U_{o1} = E \cdot \frac{R_{o1} \parallel R_g}{(R_{o1} \parallel R_g) + R_{o2}} \end{cases} \quad (1)$$

Where $R_{o1} \parallel R_g = \frac{R_{o1} \cdot R_g}{R_{o1} + R_g}$.

The relative error caused by the meter could then be expressed as:

$$\frac{U_{s1} - U_{o1}}{U_{s1}} = \frac{R_{o2}}{R_{o1} + R_{o2}} \cdot \frac{R_{o1} \parallel R_g}{R_{o1} \parallel R_g + R_{o2}} = \frac{1}{1 + \frac{R_g}{R_{o1} \parallel R_{o2}}}$$

Based on the analysis above, it can be seen that the error caused by the meter is related not only to R_g , but also to $R_{o1} \parallel R_{o2}$. The larger the value of $\frac{R_g}{R_{o1} \parallel R_{o2}}$ is, the smaller the error caused by the meter is.

Random error:

The uncertainty of the measurement results could be calculated with the following equation:

$$u_{U_0} = \left[\left(\frac{r_2}{r_1 + r_2} \cdot u_{U_{i0}} \right)^2 + \left(\frac{r_1}{(r_1 + r_2)^2} \cdot u_{r_2} \right)^2 + \left(\frac{r_2}{(r_1 + r_2)^2} \cdot u_{r_1} \right)^2 \right]^{1/2} \quad (2)$$

To correct random error, a calibration curve is recommended to compensate the error.

Materials

Instrument check

skipped.

Design a multi-range DC voltmeter

Requirements: design and construct a multi-range DC voltmeter with a range of $0 - 200mV$, $0 - 2V$, $0 - 20V$, $0 - 200V$ and $0 - 1000V$, show related R_1, R_2 values, and the corresponding measurement range.

Error analysis

Requirements: analyze the difference between the measurement results of the assembled meter and the a given voltmeter, and calculate the error caused by the meter.

Calibration curve

Requirements: record a calibration curve for the assembled meter, and use it to correct the random error.

Results

Design a multi-range DC voltmeter

range	200mv	2v	20v	200v	2000v
R_1	100kΩ	10kΩ	1kΩ	0.1kΩ	0.01kΩ
R_2	0kΩ	90kΩ	99kΩ	99.9kΩ	99.99kΩ

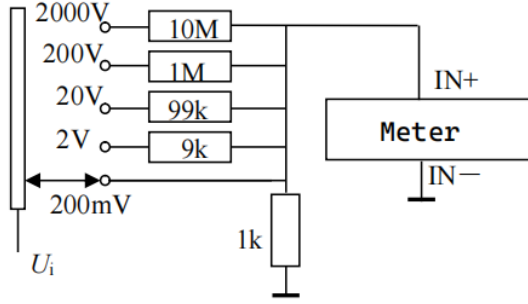


Figure 3: Multi-range DC voltmeter

The circuit is shown as Figure.3, the max range is $100k\Omega * 0.07A = 7kV$

Error analysis

$$R_1 = 10k\Omega, R_2 = 90k\Omega, R_g = 100k\Omega, U = 5V$$

The results are shown as:

$R_{o1} = R_{o2}(\Omega)$	100	500	1k	5k
$U_{s1}(V)$	2.522	2.526	2.524	2.524
$U_{o1}(V)$	2.517	2.514	2.510	2.458
$R_{o1} = R_{o2}(\Omega)$	10k	20k	40k	60k
$U_{s1}(V)$	2.521	2.522	2.517	2.514
$U_{o1}(V)$	2.399	2.289	2.100	1.937
$R_{o1} = R_{o2}(\Omega)$	80k	100k	1M	2M
$U_{s1}(V)$	2.512	2.509	2.444	2.310
$U_{o1}(V)$	1.798	1.679	0.422	0.229

Calibration curve

R_{o1}	0	20	40	60	80	100	120	140	160	180	200
R_{o2}	500	480	460	440	420	400	380	360	340	320	300
U_{s1}	0	0.2032	0.4062	0.6093	0.8122	1.0151	1.2170	1.4197	1.6227	1.8254	1.9269
U_{o1}	0	0.2011	0.4023	0.6036	0.8047	1.0057	1.2057	1.4066	1.6077	1.8087	1.9093

* Images are shown in seprate page.

References

Most contents were translated from the handout.

Acknowledgements

This is the last experiment of this course, and perhaps the last physics experiment I'll ever have in USTC. There was time I really hate this course, as most of the experiments were boring and just meaningless repeats, but by the end of this course, I really enjoy the experiments and learned a lot from it, I learned how to use latex, how to use python, I learned how to analyze data and make beautiful charts.

I would take this chance to thank all the teachers and TAs for your amazing job, and for those who offered help and encouragement, my sincere and hearty thanks and appreciations goes to all of you.

Images

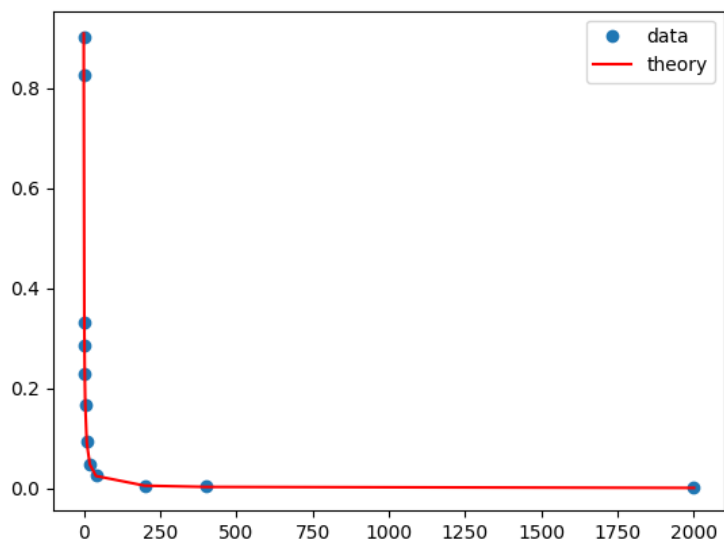


Figure 4: Error analysis

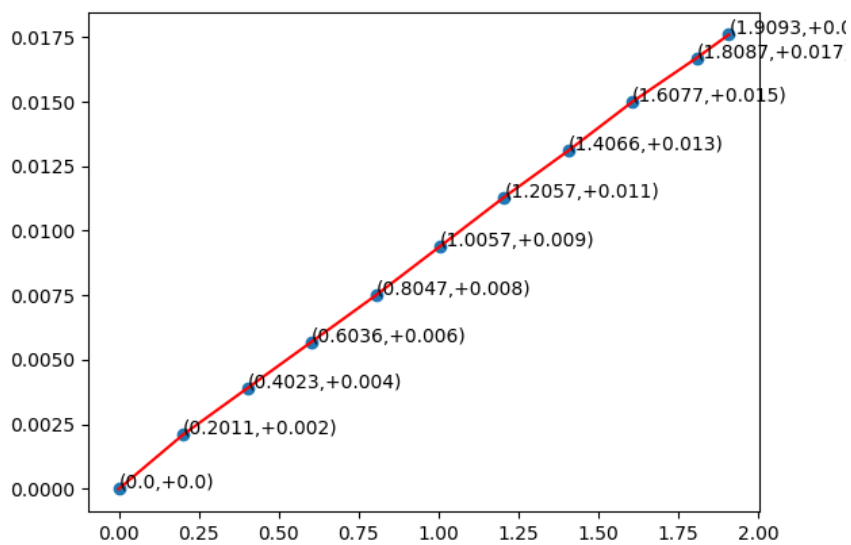


Figure 5: Calibration curve